

Name: \_\_\_\_\_

Period: \_\_\_\_\_ Table: \_\_\_\_\_



**Solve** for the missing variable **AND** for the **Power** for each circuit. [1 point ea]

**Equations**

$$V = IR$$

$$P = IV$$

